 


## Example VHDL Entity - 0 to 9 Counter



- Define input & output ports

Port Name	Direction	Bus	MSB	LSB
clk	in	<input type="checkbox"/>		
Reset	in	<input type="checkbox"/>		
Count	out	<input checked="" type="checkbox"/>	3	0
Carry	out	<input type="checkbox"/>		

## VHDL Model

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter is
Port(clk : in STD_LOGIC;
      Reset : in STD_LOGIC;
      Count : out STD_LOGIC_VECTOR (3 downto 0);
      Carry : out STD_LOGIC);
end Counter;

architecture Behavioral of Counter is
signal count_int : std_logic_vector(3 downto 0);
-- define internal register
begin

process (reset, clk)
begin
    if reset = '1' then
        count_int <= "0000"; -- set counter, and
        carry <= '0'; -- carry to zero
    elsif clk'event and clk = '1' then
        if count_int <= "1000" then -- check count
            count_int <= count_int + "1"; --increment
            carry <= '0'; -- show still below 9
        else -- else we are at 9
            count_int <= "0000"; -- roll over count
            carry <= '1'; -- flag roll over
        end if;
    end if;
end process;
count <= count_int; -- send value to the outside

end Behavioral;
```

## VHDL Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY Counter_TB IS
END Counter_TB;

ARCHITECTURE behavior OF Counter_TB IS

-- Component Declaration for UUT)
COMPONENT Counter
PORT(
    clk : IN std_logic;
    Reset : IN std_logic;
    Count : OUT std_logic_vector(3 downto 0);
    Carry : OUT std_logic );
END COMPONENT;

--Inputs
signal clk : std_logic := '0';
signal Reset : std_logic := '0';

--Outputs
signal Count : std_logic_vector(3 downto 0);
signal Carry : std_logic;

-- Clock period definitions
constant clk_period : time := 50 us; -- = 20KHz

BEGIN
-- Instantiate the Unit Under Test (UUT)
uut: Counter PORT MAP (
    clk => clk,
    Reset => Reset,
    Count => Count,
    Carry => Carry );

clk_process :process -- Clock process definitions
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

setup : PROCESS -- generate short reset pulse
BEGIN
    reset <= '0';
    wait for 3 ns;
    reset <= '1';
    wait for 3 ns;
    reset <= '0';
    wait;
end PROCESS;

END;
```

